

# Computer Aided Design CAD

---


## LECTURE 2

# Reduced incidence matrix

- Any node of a connected graph can be selected as a reference node.
- Then the voltages of the other nodes (referred to as buses) can be measured with respect to the assigned reference.

$$A = \begin{bmatrix} -1 & 1 & 0 & -1 & 0 & 0 \\ 0 & -1 & 1 & 0 & 1 & 0 \\ 1 & 0 & -1 & 0 & 0 & 1 \\ 0 & 0 & 0 & 1 & -1 & -1 \end{bmatrix}$$
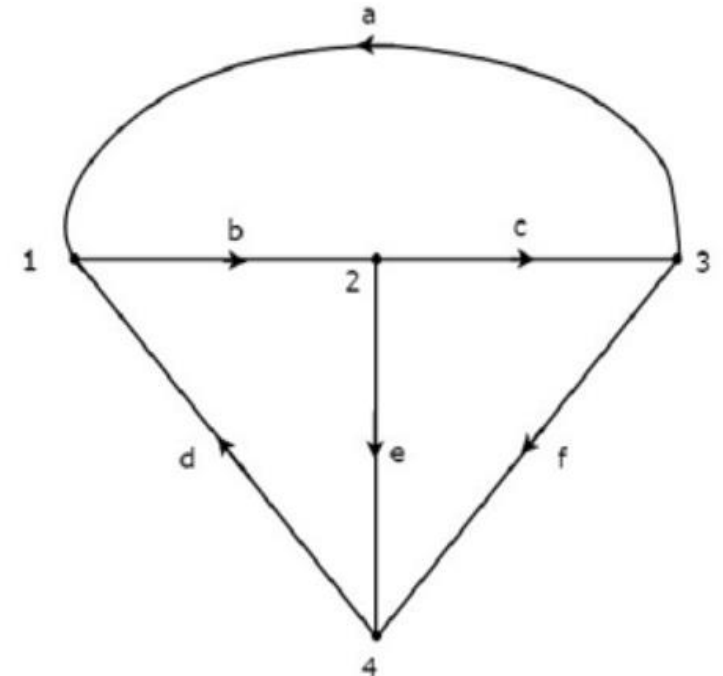
$$A = \begin{bmatrix} -1 & 1 & 0 & -1 & 0 & 0 \\ 0 & -1 & 1 & 0 & 1 & 0 \\ 1 & 0 & -1 & 0 & 0 & 1 \end{bmatrix}$$



# Apply Electrical Laws

□ From incidence matrix (A) we can apply KCL.


$$\mathbf{A} * \mathbf{J}_B = \mathbf{0}$$

$$\begin{bmatrix} a & b & c & d & e & f \\ -1 & 1 & 0 & -1 & 0 & 0 \\ 0 & -1 & 1 & 0 & 1 & 0 \\ 1 & 0 & -1 & 0 & 0 & 1 \end{bmatrix} * \begin{bmatrix} j_a \\ j_b \\ j_c \\ j_d \\ j_e \\ j_f \end{bmatrix} = 0$$

$$-j_a + j_b - j_d = 0$$

$$-j_b + j_c + j_e = 0$$

$$j_a - j_c - j_f = 0$$

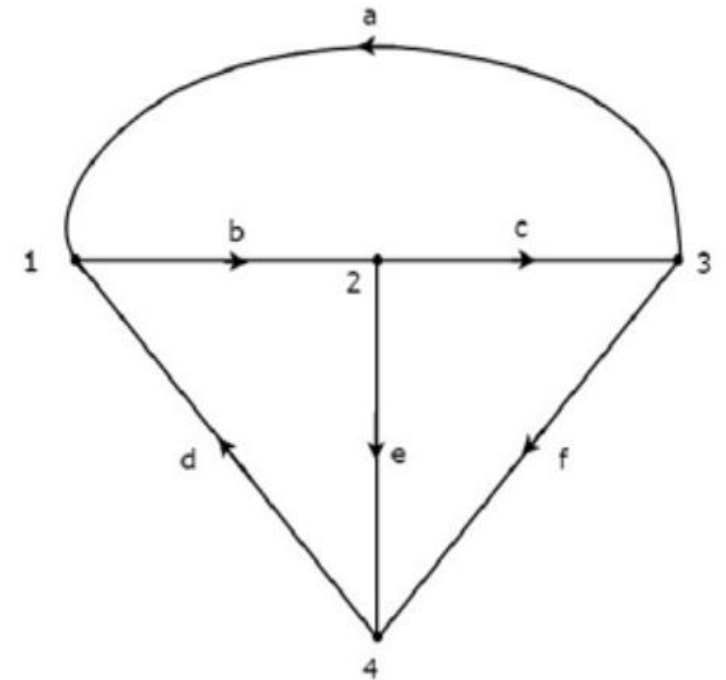

# Apply Electrical Laws

From tie set matrix (B) we can apply KVL.


$$\mathbf{B} * \mathbf{V}_B = 0$$

$$\begin{array}{cccccc} d & e & f & a & b & c \\ \begin{bmatrix} -1 & 0 & -1 & 1 & 0 & 0 \\ 1 & 1 & 0 & 0 & 1 & 0 \\ 0 & -1 & 1 & 0 & 0 & 1 \end{bmatrix} & * & \begin{bmatrix} v_d \\ v_e \\ v_f \\ v_a \\ v_b \\ v_c \end{bmatrix} & = & 0 \end{array}$$

$$-v_d - v_f + v_a = 0$$

$$v_d + v_e + v_b = 0$$

$$-v_e + v_f + v_c = 0$$

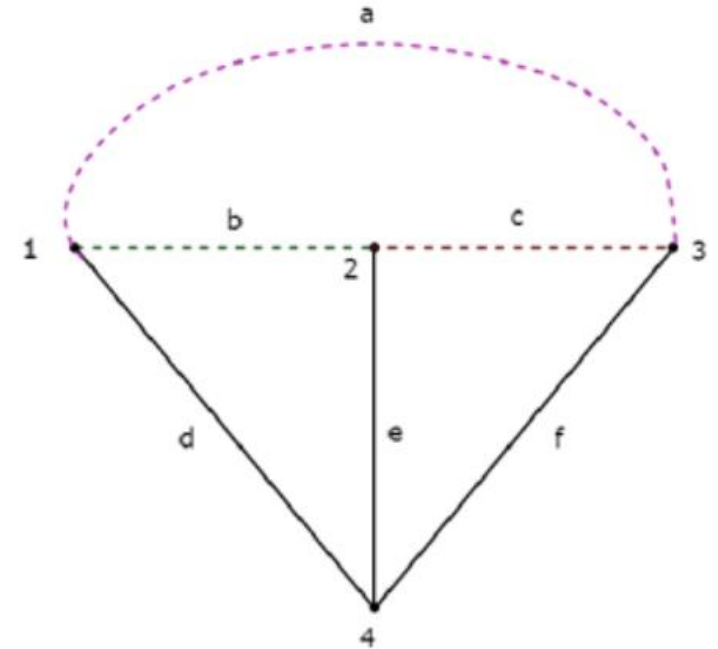

# Apply Electrical Laws


---

- Also, we can express branch currents in terms of loop currents.

$$J_B = B^T * I_L$$

Where  $J_B$  are branches current

Where  $I_L$  are loop current

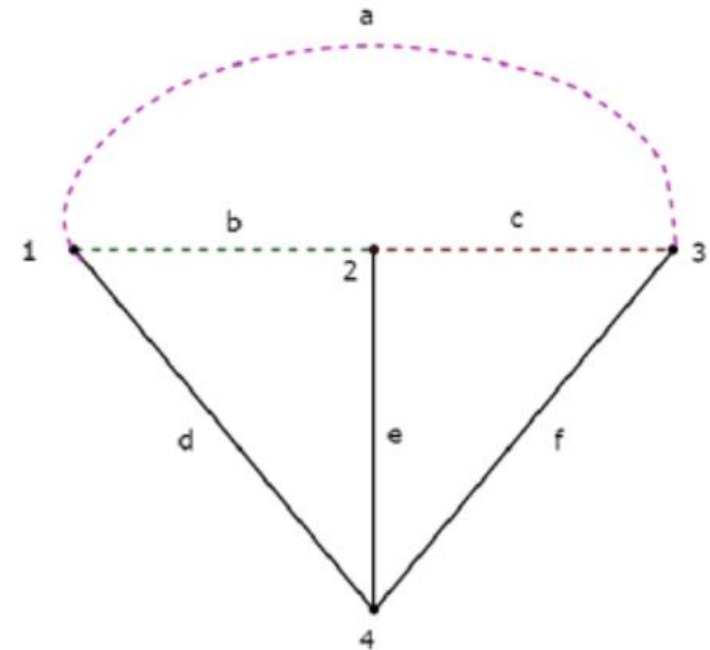

# Relation between Network Topology Matrices

---

$$C_L = -B_T^t$$

$$C_L = A_T^{-1} * A_L$$

$$C = A_T^{-1} * A$$

# Example

---

□ From A matrix calculate the B and C matrices and verify your answer by mean of obtained graph

$$A = \begin{bmatrix} -1 & 1 & 1 & 1 & 0 \\ 0 & 0 & 0 & -1 & 0 \\ 1 & -1 & 0 & 0 & -1 \end{bmatrix}$$